


Lab 2 Multiplexers, Design Hierarchy, and HEX Displays

Shi Ran 1004793495

October 1, 2020


Part II

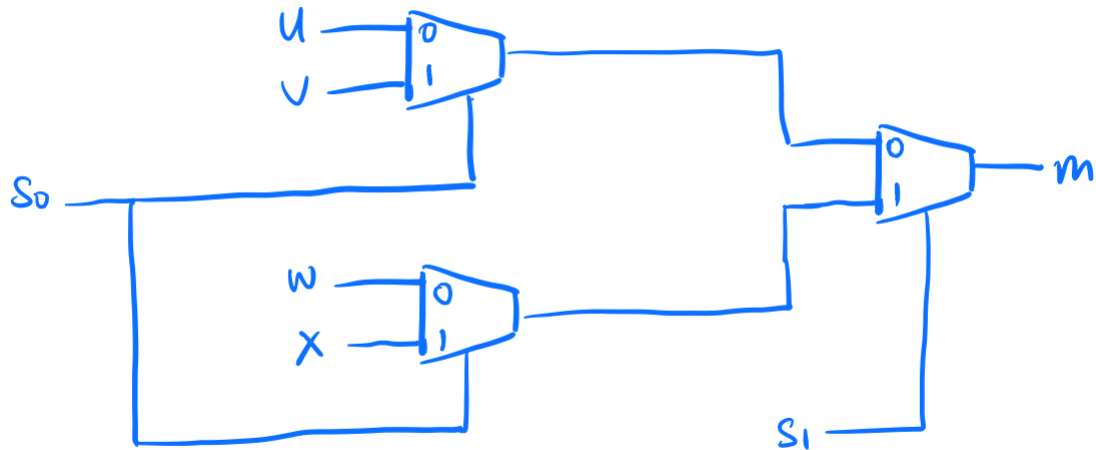1. 6 variables are needed, so there will be $2^6 = 64$ rows.
2. We can use three *mux2to1* to connect a 4-to-1 multiplexer.



In this design, s_0 decides the output of the two multiplexers on the left, s_1 decides the output of m .

- 3.

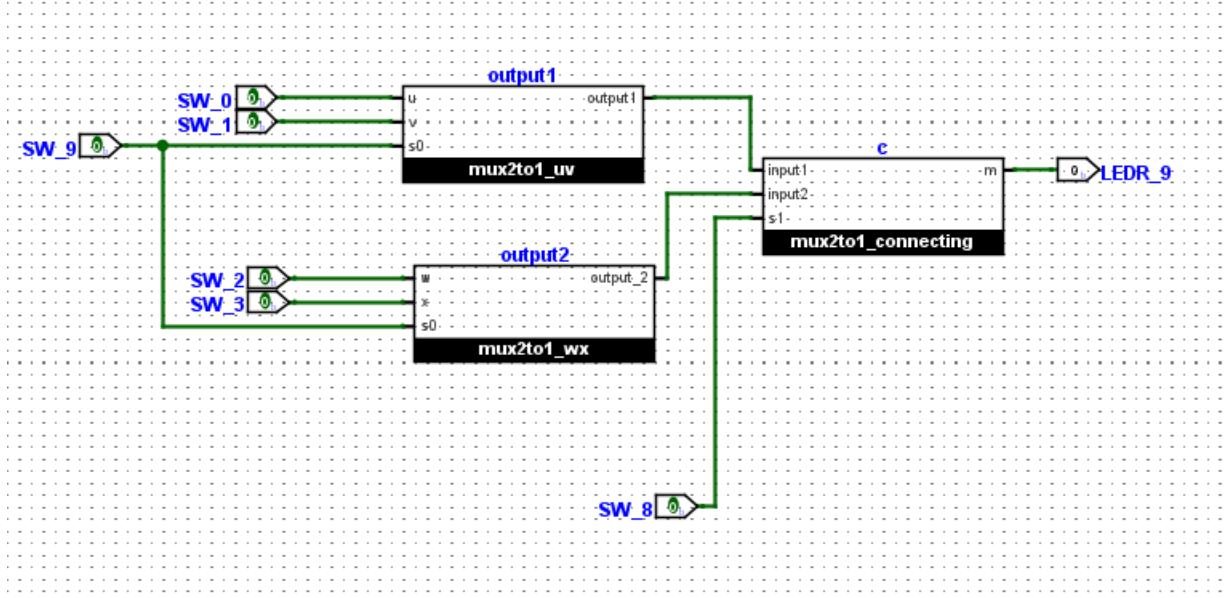

4. if $s_1s_0 = 00$, output value is determined by u , if $s_1s_0 = 01$, output value is determined by v , if $s_1s_0 = 10$, output value is determined by w , if $s_1s_0 = 11$, output value is determined by x .
- 5.

Component to FPGA board mapping

Unmapped Components:

Mapped Components:

Command:

PIN: /LEDR_9#LED0
PIN: /SW_0#Button0
PIN: /SW_1#Button0
PIN: /SW_2#Button0
PIN: /SW_3#Button0
PIN: /SW_8#Button0
PIN: /SW_9#Button0

Release component

Release all components


Load Map

Save Map

Cancel

Done

No messages

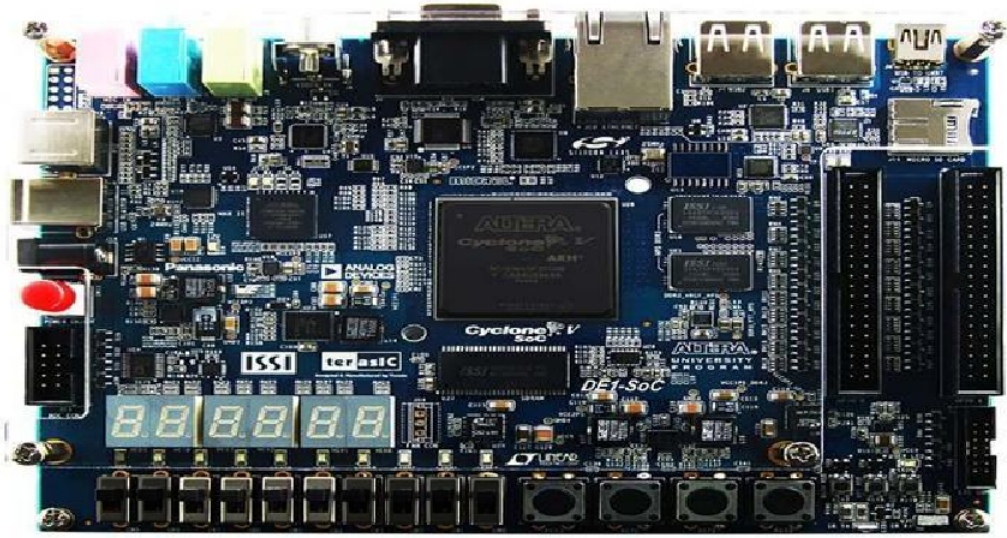

3

Part III

1. segment 0 truth table:

z	y	x	w	HEX[0]
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

Karnaugh Map:

	$\bar{x} * \bar{w}$	$\bar{x} * w$	$x * w$	$x * \bar{w}$
$\bar{z} * \bar{y}$	1	0	1	1
$\bar{z} * y$	0	1	1	1
$z * y$	1	0	1	1
$z * \bar{y}$	1	1	0	1

output: $u = x'y'z + w'y'z' + wyz' + xz' + xy + w'z$

segment 1 truth table:

z	y	x	w	HEX[1]
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

Karnaugh Map:

	$\bar{x} * \bar{w}$	$\bar{x} * w$	$x * w$	$x * \bar{w}$
$\bar{z} * \bar{y}$	1	1	1	1
$\bar{z} * y$	1	0	1	0
$z * y$	0	1	0	0
$z * \bar{y}$	1	1	0	1

output: $u = w'x'z' + wxz' + w'y'z + y'z' + wx'z$

segment 2 truth table:

z	y	x	w	HEX[2]
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

Karnaugh Map:

	$\bar{x} * \bar{w}$	$\bar{x} * w$	$x * w$	$x * \bar{w}$
$\bar{z} * \bar{y}$	1	1	1	0
$\bar{z} * y$	1	1	1	1
$z * y$	0	1	0	0
$z * \bar{y}$	1	1	1	1

output: $u = x'z' + wz' + yz' + x'w + y'z$

segment 3 truth table:

z	y	x	w	HEX[3]
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Karnaugh Map:

	$\bar{x} * \bar{w}$	$\bar{x} * w$	$x * w$	$x * \bar{w}$
$\bar{z} * \bar{y}$	1	0	1	1
$\bar{z} * y$	0	1	0	1
$z * y$	1	1	0	1
$z * \bar{y}$	1	1	1	0

output: $u = wx'y + wxy' + x'z + w'y'z' + w'xy$

segment 4 truth table:

z	y	x	w	HEX[4]
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Karnaugh Map:

	$\bar{x} * \bar{w}$	$\bar{x} * w$	$x * w$	$x * \bar{w}$
$\bar{z} * \bar{y}$	1	0	0	1
$\bar{z} * y$	0	0	0	1
$z * y$	1	1	1	1
$z * \bar{y}$	1	0	1	1

output: $u = w'x + yz + xz + w'x'y'$

segment 5 truth table:

z	y	x	w	HEX[5]
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

Karnaugh Map:

	$\bar{x} * \bar{w}$	$\bar{x} * w$	$x * w$	$x * \bar{w}$
$\bar{z} * \bar{y}$	1	0	0	0
$\bar{z} * y$	1	1	0	1
$z * y$	1	0	1	1
$z * \bar{y}$	1	1	1	1

output: $u = w'x' + x'yz' + y'z + w'y + xz$

segment 6 truth table:

z	y	x	w	HEX[6]
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


Karnaugh Map:

	$\bar{x} * \bar{w}$	$\bar{x} * w$	$x * w$	$x * \bar{w}$
$\bar{z} * \bar{y}$	0	0	1	1
$\bar{z} * y$	1	1	0	1
$z * y$	0	1	1	1
$z * \bar{y}$	1	1	1	1


output: $u = x'yz' + w'x + y'z + xy' + wz$.




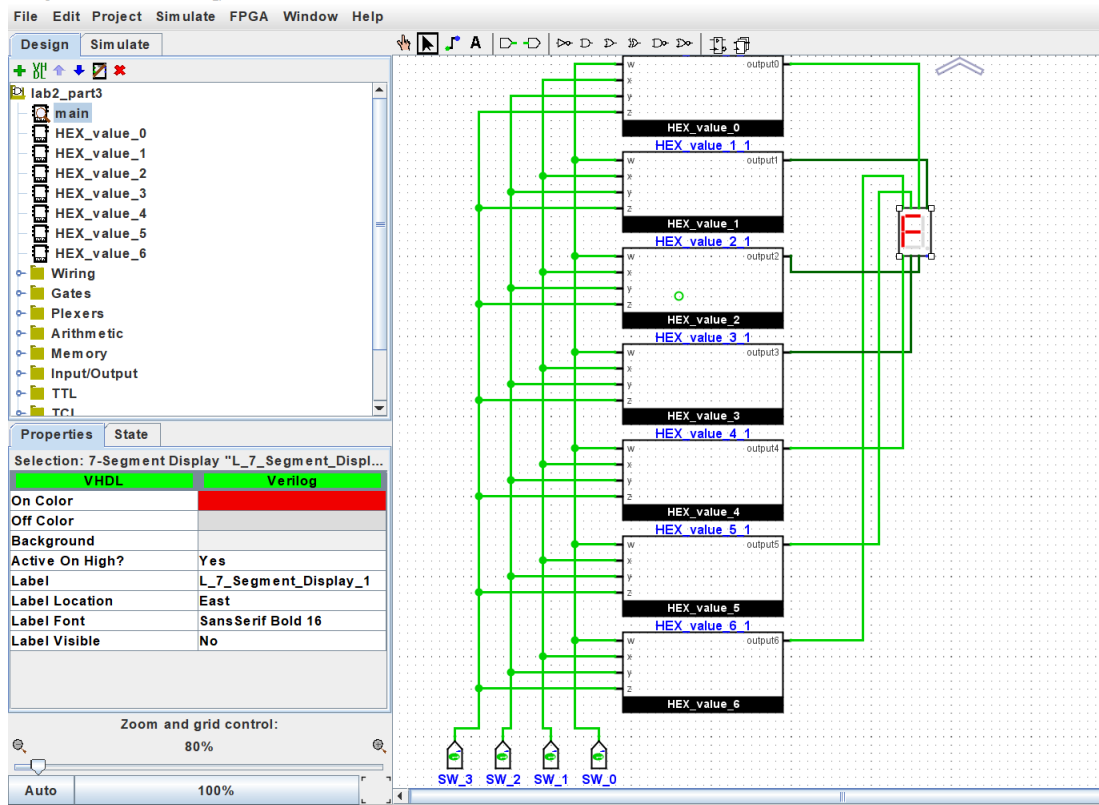
2.

Logisim-evolution: main of lab2_part3 (v 3.3.0)



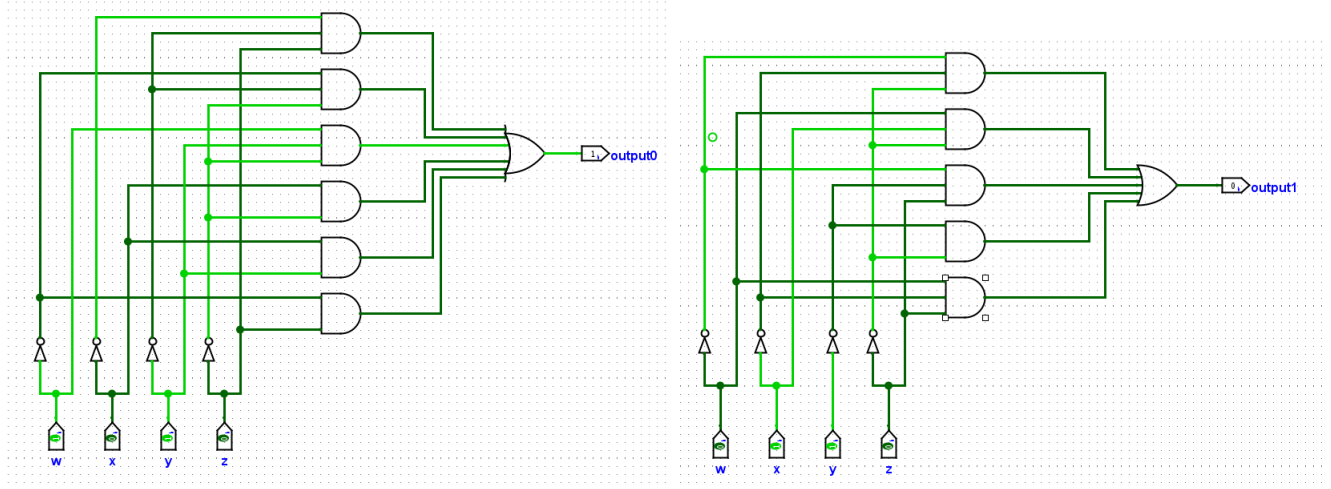Below are circuit for each HEX value, respectively.



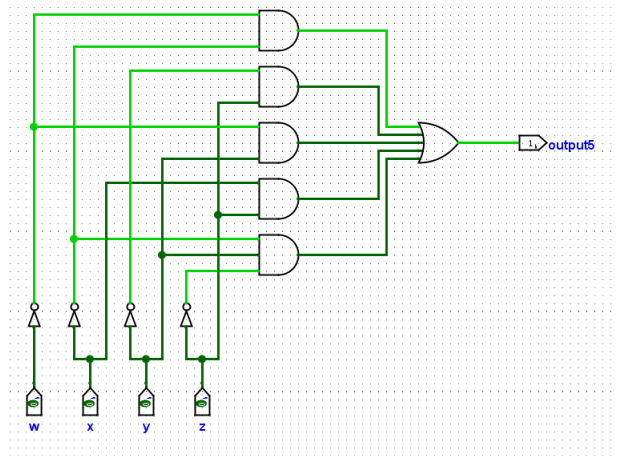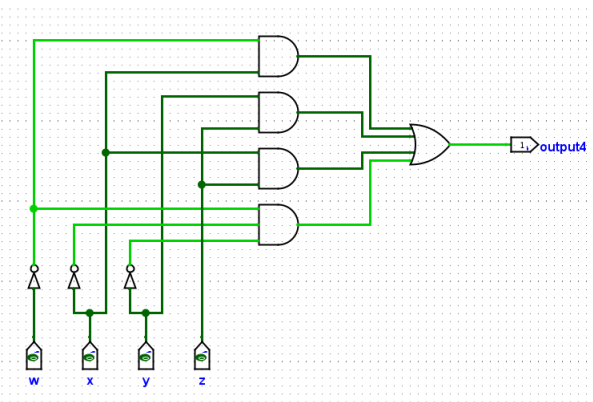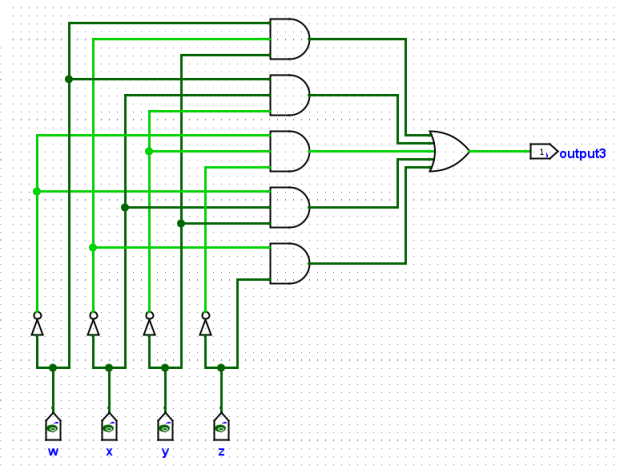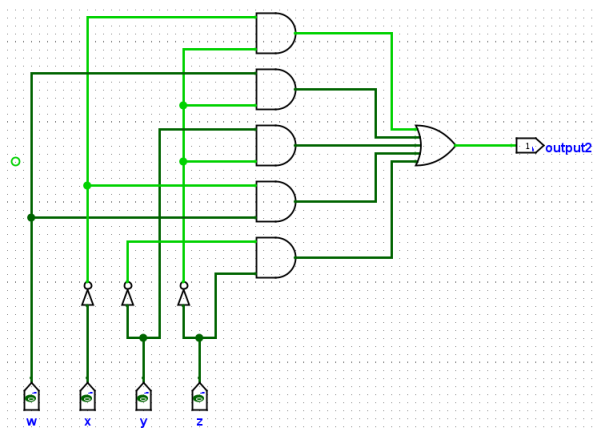

3. The followings are the screenshots of test vectors for each module, respectively.

Logisim: Test Vector HEX_value_0 of lab...

Passed: 16 Failed: 0

status	z	y	x	w	output0
pass	0	0	0	0	1
pass	0	0	0	1	0
pass	0	0	1	0	1
pass	0	0	1	1	1
pass	0	1	0	0	0
pass	0	1	0	1	1
pass	0	1	1	0	1
pass	0	1	1	1	1
pass	1	0	0	0	1
pass	1	0	0	1	1
pass	1	0	1	0	1
pass	1	0	1	1	0
pass	1	1	0	0	1
pass	1	1	0	1	0
pass	1	1	1	0	1
pass	1	1	1	1	1

Load Vector Run Stop Reset

Logisim: Test Vector HEX_value_1 of lab...

Passed: 16 Failed: 0

status	z	y	x	w	output1
pass	0	0	0	0	1
pass	0	0	0	1	1
pass	0	0	1	0	1
pass	0	0	1	1	1
pass	0	1	0	0	1
pass	0	1	0	1	0
pass	0	1	1	0	0
pass	0	1	1	1	1
pass	1	0	0	0	1
pass	1	0	0	1	1
pass	1	0	1	0	1
pass	1	0	1	1	0
pass	1	1	0	0	0
pass	1	1	0	1	1
pass	1	1	1	0	0
pass	1	1	1	1	0

Load Vector Run Stop Reset

Logisim: Test Vector HEX_value_2 of lab...

Passed: 16 Failed: 0

status	z	y	x	w	output2
pass	0	0	0	0	1
pass	0	0	0	1	1
pass	0	0	1	0	0
pass	0	0	1	1	1
pass	0	1	0	0	1
pass	0	1	0	1	1
pass	0	1	1	0	1
pass	0	1	1	1	1
pass	1	0	0	0	1
pass	1	0	0	1	1
pass	1	0	1	0	1
pass	1	0	1	1	1
pass	1	1	0	0	0
pass	1	1	0	1	1
pass	1	1	1	0	0
pass	1	1	1	1	0

Load Vector Run Stop Reset

Logisim: Test Vector HEX_value_3 of lab...

Passed: 16 Failed: 0

status	z	y	x	w	output3
pass	0	0	0	0	1
pass	0	0	0	1	0
pass	0	0	1	0	1
pass	0	0	1	1	1
pass	0	1	0	0	0
pass	0	1	0	1	1
pass	0	1	1	0	1
pass	0	1	1	1	0
pass	1	0	0	0	1
pass	1	0	0	1	1
pass	1	0	1	0	0
pass	1	0	1	1	1
pass	1	1	0	0	1
pass	1	1	0	1	1
pass	1	1	1	0	1
pass	1	1	1	1	0

Load Vector Run Stop Reset

Logisim: Test Vector HEX_value_4 of lab...

Passed: 16 Failed: 0

status	z	y	x	w	output4
pass	0	0	0	0	1
pass	0	0	0	1	0
pass	0	0	1	0	1
pass	0	0	1	1	0
pass	0	1	0	0	0
pass	0	1	0	1	0
pass	0	1	1	0	1
pass	0	1	1	1	0
pass	1	0	0	0	1
pass	1	0	0	1	0
pass	1	0	1	0	1
pass	1	0	1	1	1
pass	1	1	0	0	1
pass	1	1	0	1	1
pass	1	1	1	0	1
pass	1	1	1	1	1

Load Vector Run Stop Reset

Logisim: Test Vector HEX_value_5 of lab...

Passed: 16 Failed: 0

status	z	y	x	w	output5
pass	0	0	0	0	1
pass	0	0	0	1	0
pass	0	0	1	0	0
pass	0	0	1	1	0
pass	0	1	0	0	1
pass	0	1	0	1	1
pass	0	1	1	0	1
pass	0	1	1	1	0
pass	1	0	0	0	1
pass	1	0	0	1	1
pass	1	0	1	0	1
pass	1	0	1	1	1
pass	1	1	0	0	1
pass	1	1	0	1	0
pass	1	1	1	0	1
pass	1	1	1	1	1

Load Vector Run Stop Reset